

2. Signals to control the read and write inputs of memory.
3. Signals to set, clear, or complement the flip-flops.
4. Signals to S_2 , S_1 , and S_0 To select a register or memory for the bus.
5. Signals to control the AC adder and logic circuit.

6.9.1.1. Control of Memory and Registers

The control inputs of the registers connected to the common bus (see figure 6.4) are:

1. Load the register (**LD**).
2. Increment the register (**INR**).
3. Clear the register (**CLR**).

Suppose that it is desired to derive the gate structure associated with the control inputs of the data register (**DR**). By scanning table 6.6, it is shown that the statements that change the content of **DR** are the following:


$D_0T_4: DR \leftarrow M[AR]$
 $D_1T_4: DR \leftarrow M[AR]$
 $D_2T_4: DR \leftarrow M[AR]$
 $D_6T_4: DR \leftarrow M[AR]$
 $D_6T_5: DR \leftarrow DR + 1$

The first four statements specify transfer of information from the memory to **DR**. The content of memory is placed on the bus and the content of the bus is transferred into **DR** by enabling its **LD** control input. The fifth statement increments the data register (**DR**) by 1. The control functions can be combined into two Boolean expressions as follows:

$$LD(DR) = (D_0 + D_1 + D_2 + D_6)T_4$$

$$INR(DR) = D_6T_5$$

Figure 6.15 shows the control gate logic associated with **DR**.

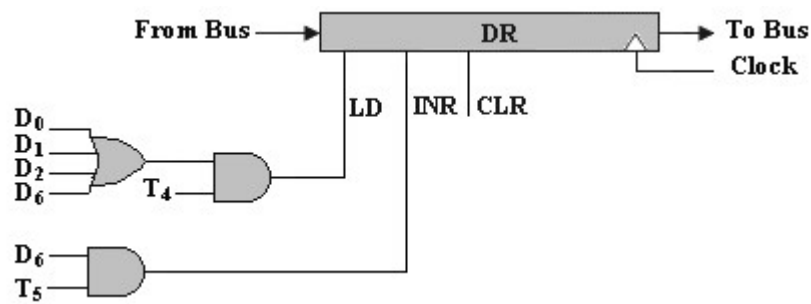
**Figure 6.15**

In similar way, one can derive the control gates for the other registers as well as the logic needed to control the read and write inputs of memory.

The logic gates associated with the write input of memory is derived by scanning table 6.6 to find the statements that specify a write operation. Note that the write operation is recognized from the symbol $M[AR] \leftarrow$.

$$Write = RT_1 + D_3T_4 + D_5T_4 + D_6T_6$$

Figure 6.16 shows the control gate logic associated with **Write** input of the memory.

 **Figure 6.16**

6.9.1.2. Control of Single Flip-Flops

In similar manner, the control gates for the seven flip-flops S, E, R, IEN, FGI, FGO, and I can be determined.

Example

Show the complete logic control of the **IEN** Flip-flop in the basic computer. Use a **JK** flip-flop for this purpose.

Solution

By scanning table 6.6, it is shown that the statements that change the state of the Flip-flop **IEN** are the following:

$$pB_7 : IEN \leftarrow 1$$

$$pB_6 : IEN \leftarrow 0$$

$$RT_2 : IEN \leftarrow 0$$

Where $p = D_7IT_3$ and B_6 and B_7 are bits 6 and 7 respectively.

Using **JK** flip-flop for the **IEN**, the complete control logic will be as shown in figure 6.17.

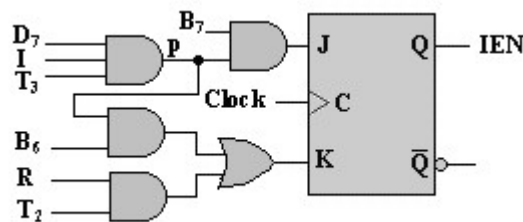


Figure 6.17

6.9.1.3. Control of Common Bus

As explained before, the 16-bit common bus is controlled by the three selection inputs S_2 , S_1 , and S_0 (see figure 6.4). To select any one of the registers or the memory, a binary number equivalent to the decimal number shown with each bus input must be applied to the selection inputs S_2 , S_1 , and S_0 in order to select the corresponding register or memory.

Table 6.7 is recognized as the truth table of a binary encoder, which specifies the binary numbers for $S_2S_1S_0$ that select each register or memory. Each binary number is associated with a Boolean variable X_1 to X_7 , corresponding to the gate structure that must be active in order to select the register or memory for the bus.

As an example, when $X_3 = 1$, the corresponding value of $S_2S_1S_0$ must be **011** and the output of **DR** will be selected for the bus.

Table 6.7

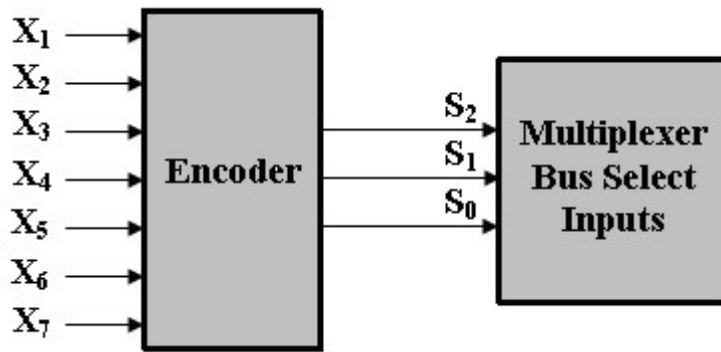
Inputs								Outputs			Selected Register for the Bus
X ₁	X ₂	X ₃	X ₄	X ₅	X ₆	X ₇	S ₂	S ₁	S ₀		
0	0	0	0	0	0	0	0	0	0	None	
1	0	0	0	0	0	0	0	0	1	AR	
0	1	0	0	0	0	0	0	0	1	PC	
0	0	1	0	0	0	0	0	0	1	DR	
0	0	0	1	0	0	0	0	1	0	AC	
0	0	0	0	1	0	0	0	1	0	IR	
0	0	0	0	0	1	0	0	1	1	TR	
0	0	0	0	0	0	1	0	1	1	Memory	

Figure 6.18 shows the encoder at the inputs of the bus selection logic. The Boolean functions for the encoder are as follows:

$$S_0 = X_1 + X_3 + X_5 + X_7$$

$$S_1 = X_2 + X_3 + X_6 + X_7$$

$$S_2 = X_4 + X_5 + X_6 + X_7$$

**Figure 6.18****How to determine the control logic for each encoder input**

Suppose that it is required to find the control logic that makes $X_2 = 1$ and $S_2S_1S_0 = 010$ (select the register PC as the source register).

We proceed as follows:

1. Scan all register transfer statements in table 6.6 and extract those statements that have PC as a source register.

$$\overline{RT}_0 : AR \leftarrow PC$$


$$RT_0 : TR \leftarrow PC$$

$$D_5T_4 : M[AR] \leftarrow PC$$

2. The Boolean function for X_2 is:

$$X_2 = \overline{RT}_0 + RT_0 + D_5T_4$$

3. Draw the control logic for X_2 (Figure 6.19).

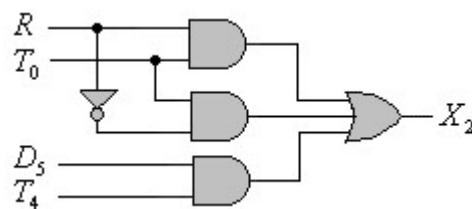**Figure 6.19**

In a similar manner, one can determine the gate logic for other registers or memory.

Homework

Find the control logic that makes $X_1 = 1$ and $S_2S_1S_0 = 001$ (select the register AR as the source register).

6.9.2. Design of Accumulator Logic

Figure 6.20 presents the circuit block diagram associated with the accumulator register (AC).

The adder and logic circuit has three inputs:

1. **16-bit** inputs from the outputs of the accumulator register (AC) it self.
2. **16-bit** inputs from the data register DR.
3. **8-bit** inputs from the input register INPR.

The output of the adder and logic circuit provides the data inputs for the accumulator register (AC).

In addition, it is necessary to include in the design the logic gates for controlling the **LD**, **INR**, and **CLR** of the register and the controlling operation of the adder and logic circuit.

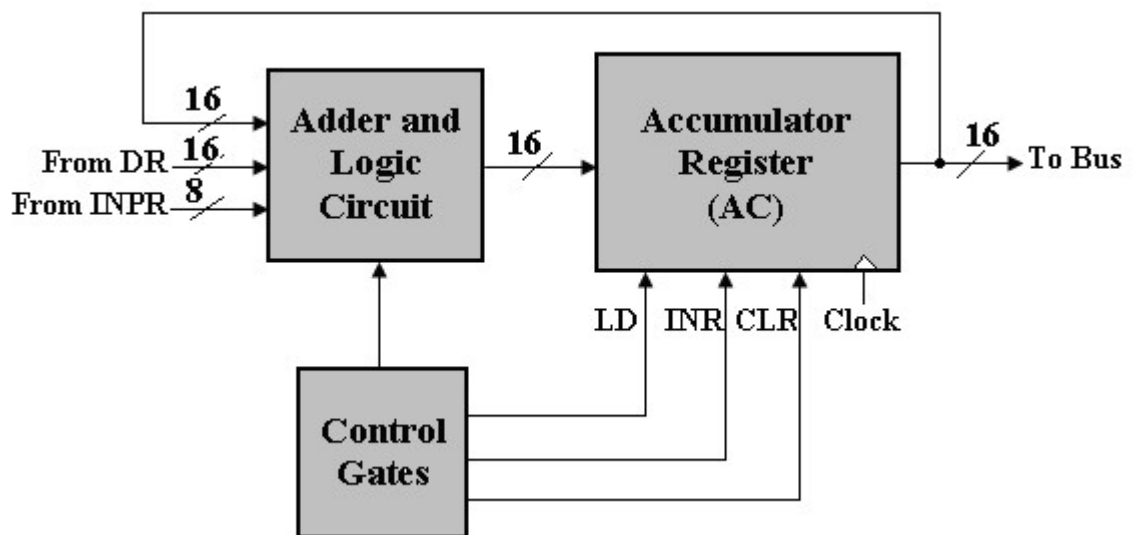


Figure 6.20

6.9.2.1. Control of Accumulator Register

In the same manner in order to design the logic that controls the accumulator register **AC**, it is necessary to scan all register transfer statements in table 6.6 and extract those statements that change the content of **AC**. These register transfer statements are:

$D_0T_5 : AC \leftarrow AC \cap DR$	<i>AND with DR</i>
$D_1T_5 : AC \leftarrow AC + DR$	<i>Add with DR</i>
$D_2T_5 : AC \leftarrow DR$	<i>Transfer from DR</i>
$pB_{11} : AC(0-7) \leftarrow INPR$	<i>Transfer from INPR</i>
$rB_9 : AC \leftarrow \overline{AC}$	<i>Complement</i>
$rB_7 : AC \leftarrow shr AC, \quad AC(15) \leftarrow E$	<i>Shift right AC</i>
$rB_6 : AC \leftarrow shl AC, \quad AC(0) \leftarrow E$	<i>Shift left AC</i>
$rB_{11} : AC \leftarrow 0$	<i>Clear AC</i>
$rB_5 : AC \leftarrow AC + 1$	<i>Increment AC</i>

From the control functions in the list above, the gate configuration is derived as follows:

1. The control function for the increment microoperation (**INR**) is rB_5 , where $r = D_7\bar{I}T_3$ and $B_5 = IR(5)$.
2. The control function for the clear microoperation (**CLR**) is rB_{11} , where $r = D_7\bar{I}T_3$ and $B_{11} = IR(11)$.
3. The control function for the load microoperation (**LD**) is the result of the remaining seven microoperations, which generated in the adder and logic circuit and are loaded at the proper time.

Figure 6.21 shows the gate structure that controls the **LD**, **INR**, and **CLR** inputs of the accumulator register **AC**. **Note that the outputs of the gates for each control function are marked with a symbolic name.**

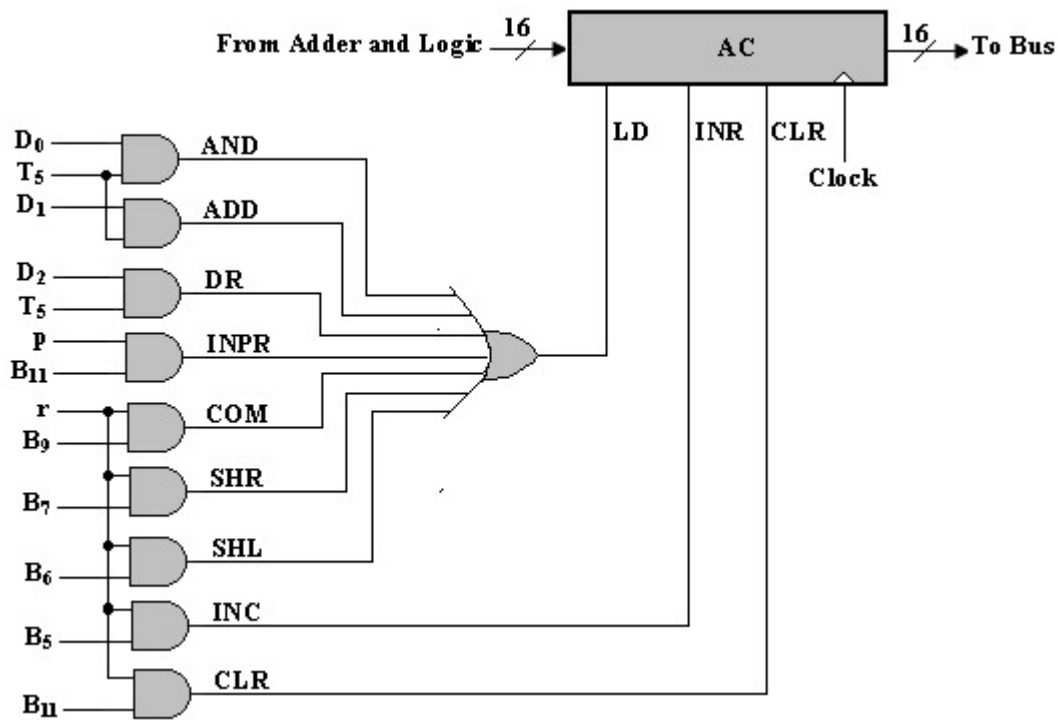


Figure 6.21

6.9.2.2. Adder and Logic Circuit

Figure 6.22 shows the internal construction of the accumulator register AC. Each stage has a JK flip-flop, two OR gates, and two AND gates. The load (LD) is connected to the inputs of the AND gates.

Figure 6.23 shows one stage of AC register (here the OR gates are removed) since the other functions (i.e. Clear and Increment of the register AC are not included). When LD input is enabled, the 16 inputs I_i for $i = 0, 1, 2, \dots, 14, 15$ are transferred to AC (0-15).

Every stage of Adder and Logic Circuit consists of:

1. Seven AND gates, every one has one of its inputs one of the functions comes from figure 6.21 as an enable. For example, the input named DR in figure 6.23 connected to the output marked DR in figure 6.21.
2. One OR gate.
3. One Full-adder (FA).

How the arithmetic and logic operations are achieved?

1. ADD operation

This operation achieved using a binary full-adder having their two inputs from the corresponding bits (i) of registers **AC** and **DR**, the input carry from the previous stage, and the result transfers through **OR** gate to register **AC**, and the output carry to next stage or to the **E** flip-flop when this stage is the last stage.

2. AND operation

The **AND** operation is obtained through **ANDing** **AC** (i) with the corresponding bit in the data register **DR** (i), and the result transfers through **OR** gate to register **AC**.

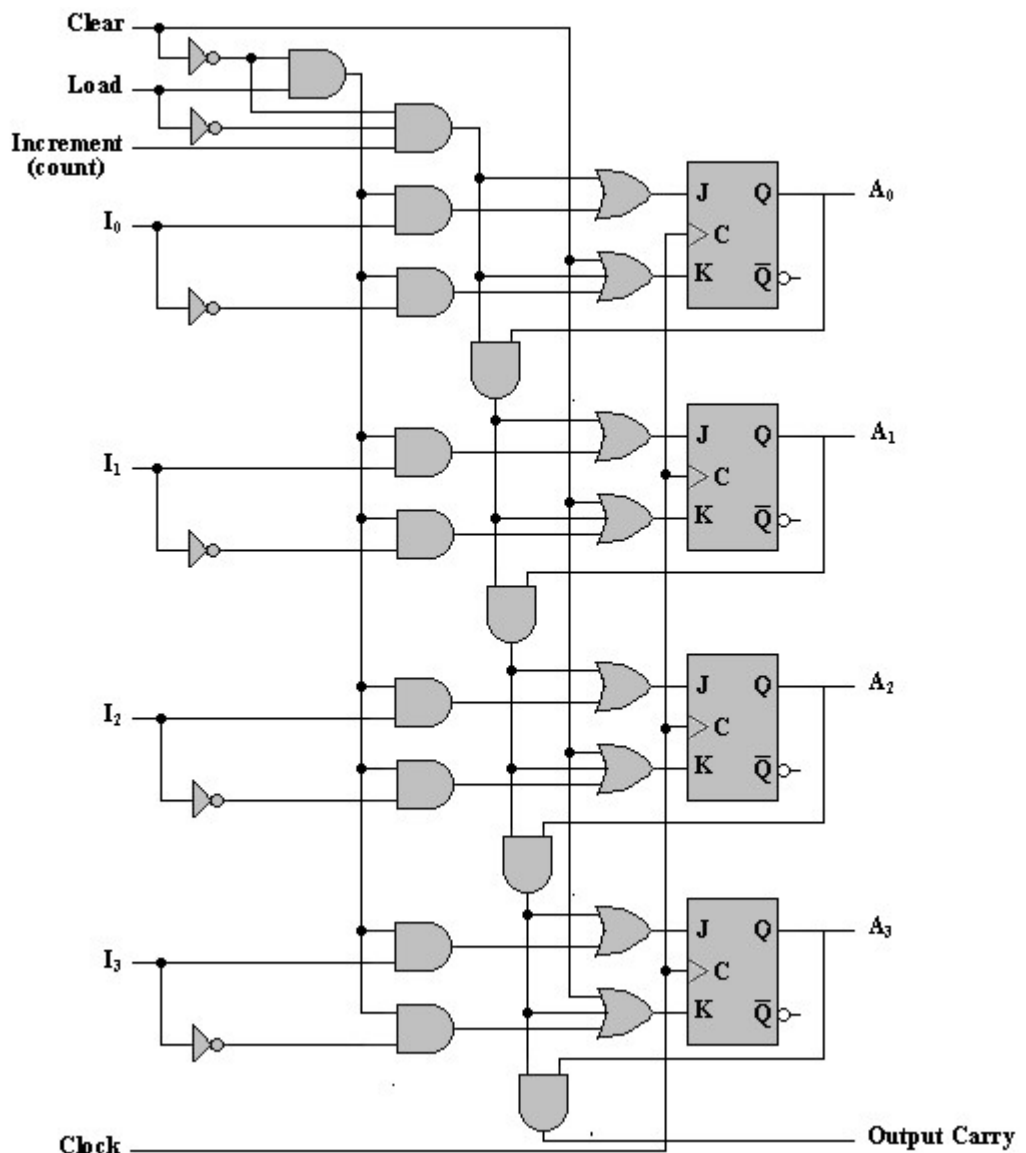


Figure 6.22

3. Transfer the content of the register DR

When DR input is active, the content of the register DR transferred to the register AC.

4. Transfer the content of the register INPR

When INPR input is active, the 8-bits of the register INPR transferred to Bits 0-7 of the accumulator register AC.

5. Complementation of the contents of AC register

When COM input is active, the content of register AC is inverted and re-transferred to the register.

6. Shift-right operation

This operation transfers bit AC ($i+1$) into bit AC (i).

7. Shift-left operation

This operation transfers bit AC ($i-1$) into bit AC (i).

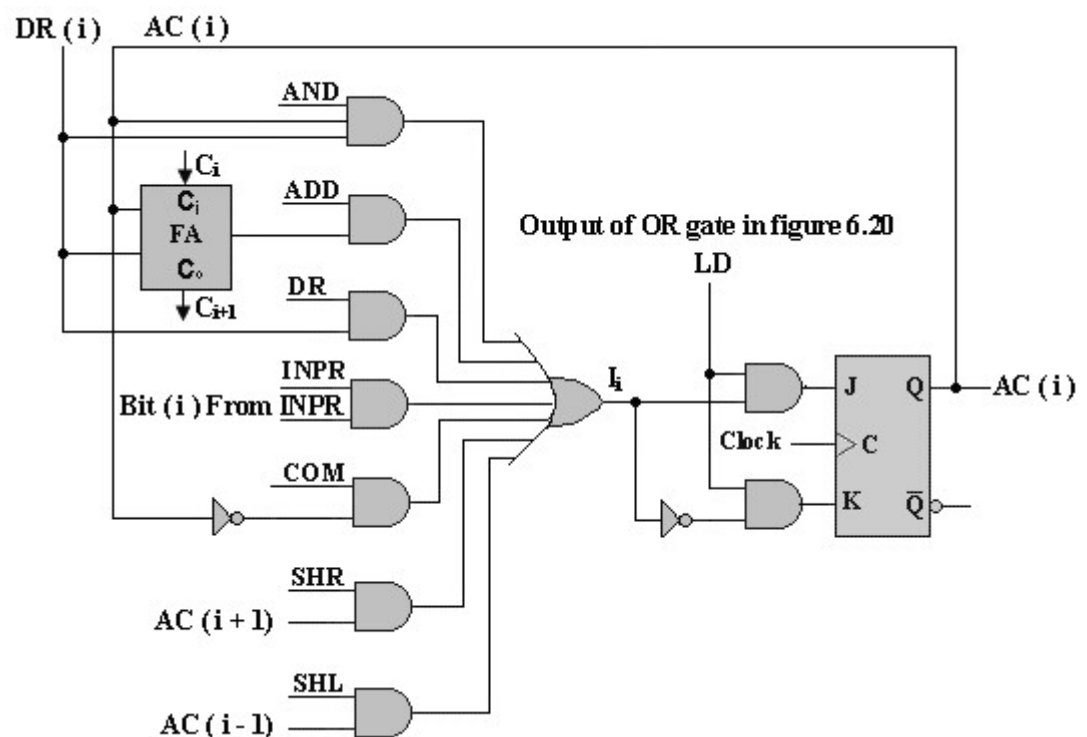


Figure 6.23

Problems of Chapter Six

- Q1.** A computer uses a memory unit with 256 words of 32 bits each. A binary instruction code is stored in one word of memory. The instruction has four parts as follows:
- Indirect bit.
 - Operation code.
 - Register code part to specify one of 64 registers.
 - Address part.
- (1) How many bits are there in:
- The operation code.
 - The register code part.
 - The address part.
- (2) Draw the instruction word format and indicate the number of bits in each part.
- (3) how many bits are there in the data and address inputs of the memory.
- Q2.** What is the difference between a direct and indirect address instruction? How many references to memory needed for each type of instructions to bring an operand into a processor register?
- Q3.** The following control inputs are active in the bus system shown in figure 6.4. For each case, specify the register transfer that will be executed during the next clock transition.

Selection Input			LD of Register	Memory	Adder
S ₁	S ₂	S ₃			
1	1	1	IR	Read	-
1	1	0	PC	-	-
1	0	0	DR	Write	-
0	0	0	AC	-	Add

- Q4.** The content of AC in the basic computer is hexadecimal A937 and the initial value of E is 1. Determine the contents of AC, E, PC, AR, and IR in hexadecimal after the execution of the CLA instruction. Repeat 11 more times, starting from each one of the registers-reference instructions. The initial value of PC is hexadecimal 021.

- Q5.** An instruction at address 021 in the basic computer has $I = 0$, an operation code of the AND instruction, and an address part equal to 083. The memory word at address 083 contains the operand B8F2 and the content of AC is A937. **Go over the instruction cycle and determine the contents of the following registers at the end of the execute phase: PC, AR, DR, AC, and IR. Repeat the problem six more times starting with an operation code of another memory-reference instruction.**
- Q6.** Show the contents in hexadecimal of registers PC, AR, DR, IR, and SC of the basic computer when an ISZ indirect instruction fetched from memory and executed. The initial content of PC is 7FF. The content of memory at address 7FF is EA9F. The content of memory at address A9F is 0C35. The content of memory at address C35 is FFFF. **Give the answer in a table with five columns, one for each register and a row for each timing signal. Show the contents of the registers after the positive transition of each clock pulse.**
- Q7.** The content of PC in the basic computer is 3AF. The content of AC is 7EC3. The content of memory at address 3AF is 932E. The content of memory at address 32E is 09AC. The content of memory at address 9AC is 8B9F.
- What is the instruction that fetched and executed next?**
 - Show the binary operation that performed in the AC when, the instruction is executed.**
 - Give the content of registers PC, AR, DR, AC, and IR in hexadecimal and the value of E, I, and the sequence counter SC in binary at the end of the instruction cycle.**

Selected problems from chapter 5 in the text for exa.

- P1.** The following control inputs are active in the bus system shown in fig. 5-4. for each case, specify the register transfer that will be executed during the next clock transition.

	S_2	S_1	S_0	LD of Register	Memory	adder
a.	1	1	1	IR	Read	-
b.	1	1	0	PC	-	-
c.	1	0	0	DR	Write	-
d.	0	0	0	AC	-	Add

- P2.** The following register transfers are to be executed in the system of fig. 5-4.

- $AR \leftarrow PC$
 - $IR \leftarrow M[AR]$
 - $M[AR] \leftarrow TR$
 - $AC \leftarrow DR, DR \leftarrow AC$
- Done simultaneously